

Ryerson University
Department of Electrical and Computer Engineering
ELE734: LOW-POWER DIGITAL INTEGRATED CIRCUITS
Mid-Term Examination, October, 2012
Duration: 1.5 hours

Student's Name: *Solution*

Student's Number: Section:

NOTES:

1. This is a **Closed Book** examination. No aids other than the approved calculators and **1 sheet (2 pages) of aid sheet** are allowed.
2. Answer all questions.
3. **No questions are to be asked** in the examination hall. If doubt exists as to the interpretation of any question, the student is urged to submit with the answer paper, a clear statement of any assumptions made.

<i>Question No.</i>	<i>Mark of each question</i>	<i>Mark obtained</i>
Q1	20	
Q2	20	
Q3	20	
Q4	20	
Total (Out of 80):		

Q1:


Design a static CMOS gate that has the following output.

$$Out = \overline{A(B+C)+DE}$$

- Draw the transistor-level schematic of your design. Size the transistors to provide a worst case pull-up and pull-down resistance of R (assuming a unit nmos transistor has the resistance of R and a unit pmos transistor has the resistance of 2R). (10 marks)
- Draw stick diagram of the gate you designed in Q1 (please clearly label metal, poly, n-diffusion and p-diffusion regions on your stick diagram). (5 marks)
- Estimate the area of the gate based on your stick diagram. (5 marks)


$$Z = \overline{A \cdot (B+C) + D \cdot E}$$

nmos network.

 


$$Z = \overline{A \cdot (B+C) + D \cdot E}$$

 
$$\begin{aligned} &= \overline{A \cdot (B+C)} \cdot \overline{D \cdot E} \\ &= (\overline{A} + \overline{B+C}) \cdot (\overline{D} + \overline{E}) \\ &= (\overline{A} + \overline{B} \cdot \overline{C}) \cdot (\overline{D} + \overline{E}) \end{aligned}$$




All together

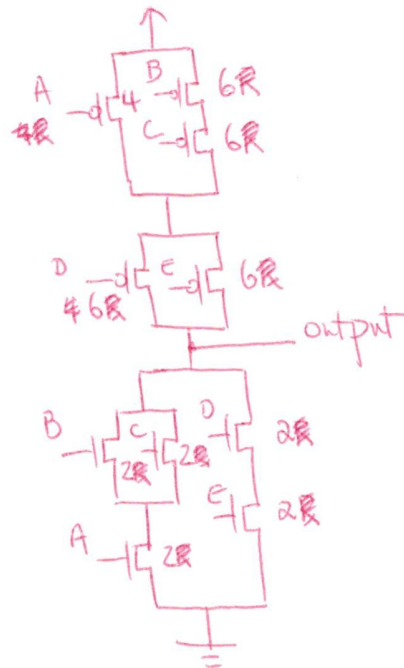

 sizing pull up 2 marks
pull down 2 marks.



Blank page

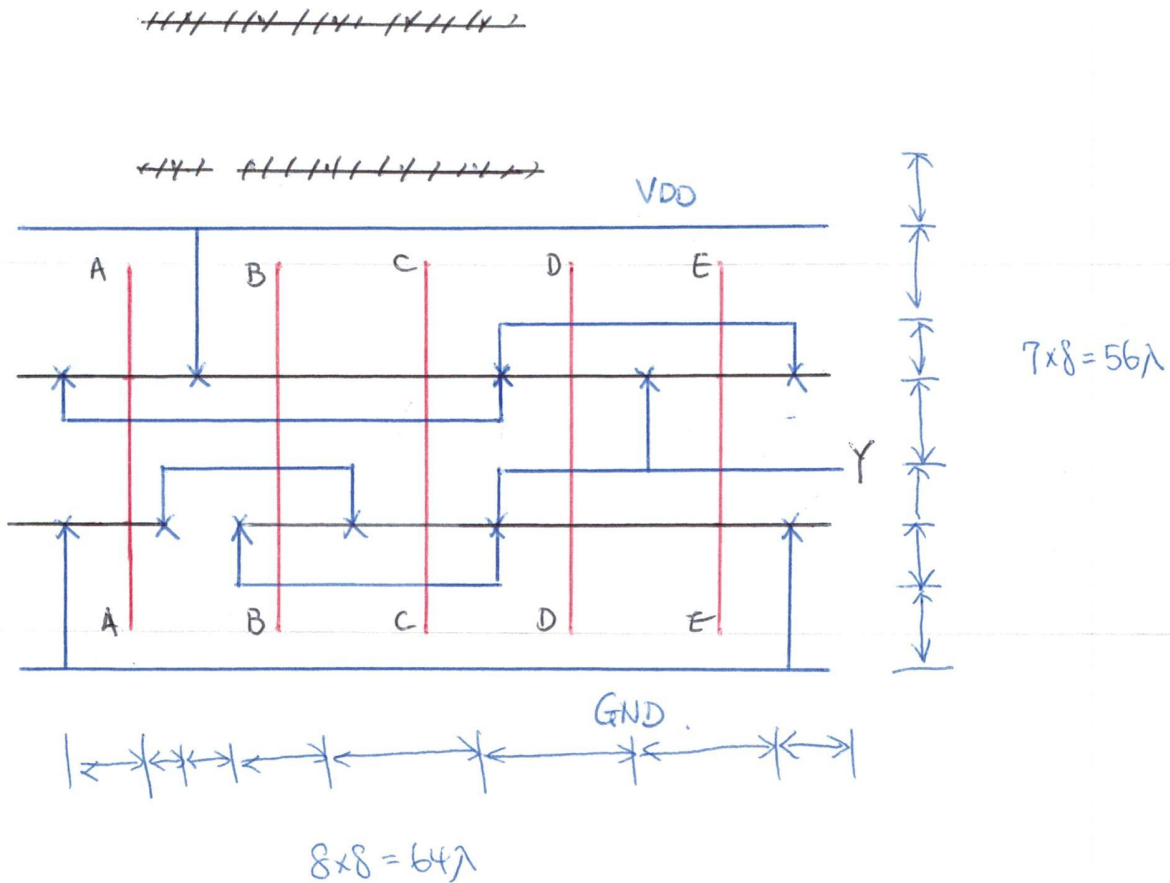

$$56 \times 64 \lambda^2 = 3584 \lambda^2$$

- +2 basic poly on diffusion layout.
- +2 no wire crossing
- +2 basic connections are correct.
- +2 horizontal dimension
- +2 vertical dimension

Q2:

- List the three I-V equations that govern the cutoff, linear, and saturation regions of operation of an ideal nMOS (long-channel/Shockley model) (10 marks).
- If one want to increase the threshold voltage through body effect, should the body voltage be increased or decreased? Why? (10 marks).

a)

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t \quad \text{cutoff} \\ \beta(V_{GT} - V_{ds}/2)V_{ds} & V_{ds} < V_{GT} \quad \text{Linear} \\ \frac{\beta}{2}V_{GT}^2 & V_{ds} > V_{GT} \quad \text{Saturation} \end{cases}$$

$$V_{GT} = V_{gs} - V_t$$

$$\beta = \mu C_{ox} \frac{W}{L}$$

← transistor width
 ← transistor length
 ↑ mobility
 ↑ gate oxide capacitance

Blank page


b) $V_t = V_{t0} + \gamma (\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s})$ ⁽⁺⁴⁾ or $V_t = V_{t0} + K_r V_{sb}$.

body voltage should be decreased ⁽⁺³⁾

because dec body voltage increases V_{sb} ⁽⁺³⁾
increases V_t

 Q3:


Calculate the worst case pull-up and pull-down logic effort and the parasitic delay of the following gate (please account for all internal diffusion capacitances in your calculations). (20 marks)



Worst case pull up

① discharge most caps. [2 marks]


 
* pmos C must be on \Rightarrow nmos C must be off \Rightarrow nmos A+B must be on \Rightarrow A=1 B=1 C=0 \Rightarrow Initial Configuration



② charge up most of discharged caps [2 marks]

* Turn B nmos off \Rightarrow turn B pmos on \Rightarrow A=1 B=0 C=0

 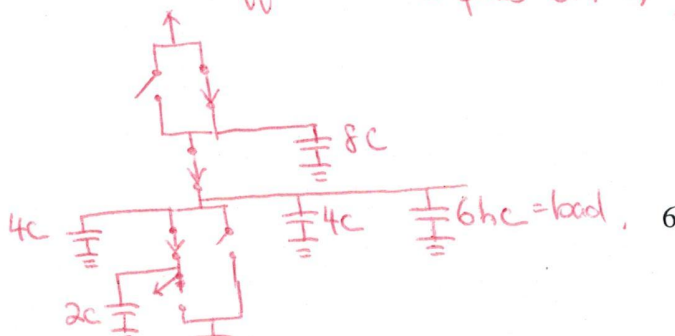Final configuration \Rightarrow B is switching load = 6hc.



Blank page

[1 mark]

parasitic delay

logic effort

$$t_{pdr}/3RC = \frac{14}{3} + 2h \quad [1 \text{ mark}]$$

$t_{pdr} =$

$$\begin{aligned} & 2C(0.5+0.5)R + 8C(0.5+0.5)R + 6hC(0.5+0.5)R + 8C \cdot 0.5R \\ &= 2RC + 8RC + 6hRC + 4RC \\ &= 14RC + 6hRC \end{aligned} \quad [2 \text{ marks}]$$

Worst case Pull down

① charge most caps [2 marks]

* pmos C must be on \Rightarrow nmos C must be off $C=0$

* A nmos must be on \Rightarrow pmos A must be off $A=1$

* B pmos must be on \Rightarrow B nmos must be off $B=0$


$A=1, B=0, C=0 \Rightarrow$ initial configuration

② discharge most of charged caps [2 marks]

* turn B pmos off \Rightarrow turn B nmos on

$A=1, B=1, C=0 \Rightarrow$ final configuration

B is switching load = $6hC$

 


[2 marks]

$t_{pdf} =$

$$\begin{aligned} & 8C(0.5+0.5)R + 8C(0.5+0.5)R + 6hC(0.5+0.5)R + 2C(0.5)R \\ &= 8RC + 8RC + 6hRC + RC \\ &= 17RC + 6hRC \end{aligned} \quad [2 \text{ marks}]$$


$$t_{pdf}/3RC = \frac{17}{3} + 2h$$

[1 mark]

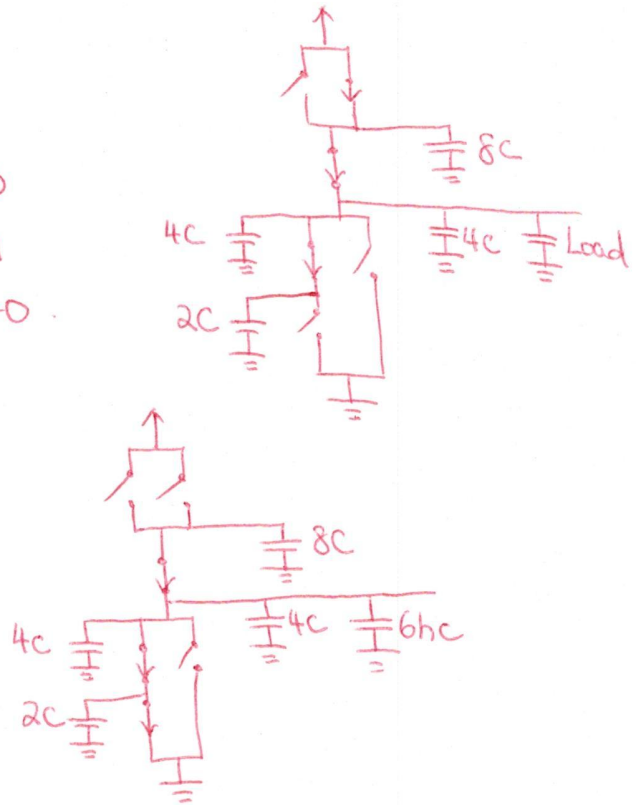

 Q4:

Calculate the optimum path delay and the transistor size for the following circuit, where C_{inv} is the input capacitance of the inverter. (inverter: $g=1, p=1$; 2-input nand: $g=4/3, p=2$; 2-input nor: $g=5/3, p=2$; 4-input nand: $g=6/3, p=4$) (20 marks)



$$h_1 = \frac{x_1}{C_{inv}} \quad h_2 = \frac{x_2}{x_1} \quad h_3 = \frac{x_3}{x_2} \quad h_4 = \frac{500C_{inv}}{x_3}$$

$$b_1 = 1 \quad b_2 = 4 \quad b_3 = 1 \quad b_4 = 1$$

$$g_1 = 1 \quad g_2 = \frac{5}{3} \quad g_3 = \frac{4}{3} \quad g_4 = \frac{6}{3}$$

$$F = GBH$$

$$= (g_1 g_2 g_3 g_4) (b_1 b_2 b_3 b_4) (h_1 h_2 h_3 h_4) \quad \underline{4 \text{ marks}}$$

$$= (1 \cdot \frac{5}{3} \cdot \frac{4}{3} \cdot \frac{6}{3}) (1 \cdot 4 \cdot 1 \cdot 1) (\frac{500C_{inv}}{C_{inv}})$$

$$= 8888.89$$

$$(F)^{1/4} = 9.71 \quad \underline{2 \text{ marks}}$$

$$\text{Optimal path delay} = 9.71 \times 4 + 1 + 2 + 2 + 4 = 47.84 \quad \underline{2 \text{ marks}}$$

$$g_1 h_1 b_1 = 9.71$$

$$1 \cdot \frac{x_1}{C_{inv}} \cdot 4 = 9.71$$

$$x_1 = 2.43 C_{inv}$$

2 marks

$$g_2 h_2 b_2 = 9.71$$

$$\frac{5}{3} \cdot \frac{x_2}{x_1} \cdot 1 = 9.71$$

$$x_2 = 14.16 C_{inv}$$

2 marks

$$g_3 h_3 b_3 = 9.71$$

$$\frac{4}{3} \cdot \frac{x_3}{x_2} \cdot 1 = 9.71$$

$$x_3 = 103.12 C_{inv}$$

2 marks

$$g_4 h_4 b_4 = 9.71$$

$$\frac{6}{3} \cdot \frac{500C_{inv}}{x_3} \cdot 1 = 9.71$$


$$500C_{inv} = 500.65 C_{inv}$$

↑


Check.

2 marks

Blank page

 


1 mark

 

1 mark

$$\frac{5}{3} C_{inv} \cdot y_1 = 2.43 C_{inv}$$


$$y_1 = 1.458$$

 

1 mark

$$\frac{4}{3} C_{inv} \cdot y_2 = 14.16 C_{inv}$$

$$y_2 = 10.62$$

 

1 mark

$$103.12 C_{inv} = \frac{6}{3} C_{inv} \cdot y_3$$

$$y_3 = 51.656$$