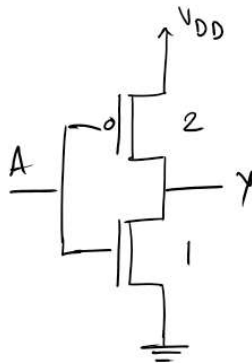


## 1. Pre-Lab


1.1.

Unskewed :

Inverter



NAND2

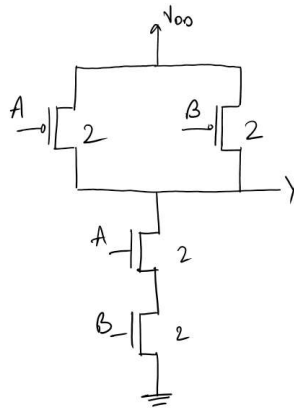

NOR2


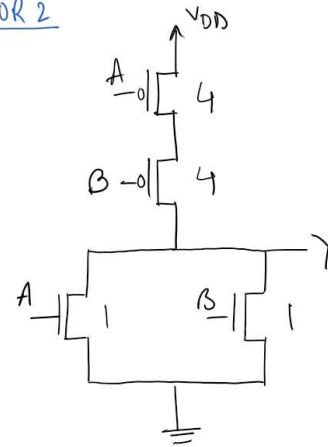



Figure 1: Unskewed Inverter, NOR2 and NAND2 gates.

Lo-skewed :

Inverter

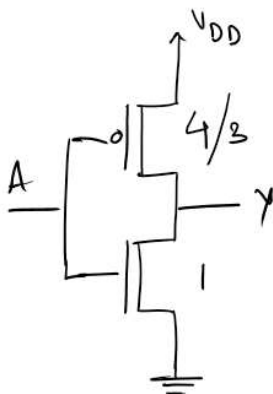

NAND2

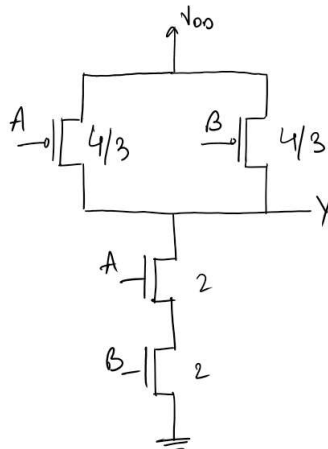

NOR2


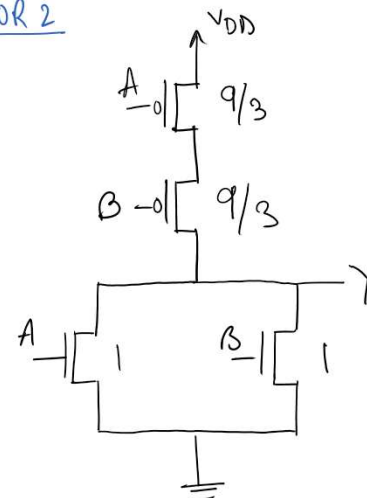



Figure 2: Low-skewed Inverter, NOR2 and NAND2 gates.

Hi-skewed:

Inverter

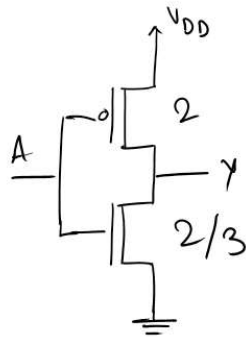

NAND 2

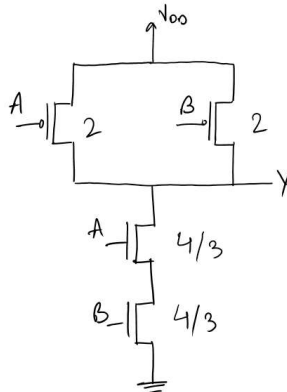

NOR 2


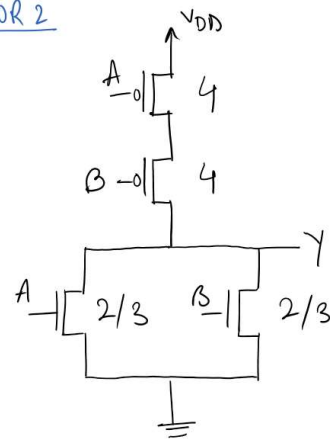


Figure 3: High-skewed Inverter, NOR2 and NAND2 gates.

## 1.2

NAND2:


Unskewed-up

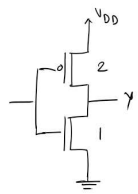

$$g_u = \frac{C_{in}}{C_{inv}} = \frac{2+2}{2+1} = \frac{4}{3}$$

$$p_u = \frac{C_{out}}{C_{inv}} = \frac{2+2+2}{2+1} = 2$$


Unskewed-down

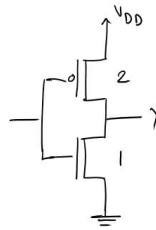

$$g_d = \frac{C_{in}}{C_{inv}} = \frac{2+2}{2+1} = \frac{4}{3}$$


$$p_d = \frac{C_{out}}{C_{inv}} = \frac{2+2+2}{2+1} = 2$$

Lo-skewed-up

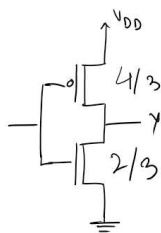

$$\frac{2R}{\frac{2R}{4/3}} = 4/3$$

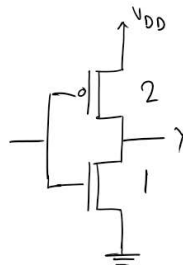
$$g_u = \frac{2 + 4/3}{4/3 + 2/3} = 1.67$$




$$\frac{R}{\frac{R \times 2}{2}} = 1$$

$$g_d = \frac{2 + 4/3}{3} = 1.11$$

Hi-skewed-up

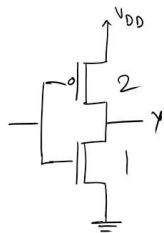

$$g_u = \frac{2 + 4/3}{3} = 1.11$$

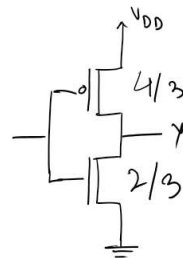

$$\frac{R}{\frac{R \times 2}{4/3}} = 2/3$$

$$g_d = \frac{2 + 4/3}{4/3 + 2/3} = 1.67$$

$$g_{avg}(\text{Unskewed}) = \frac{4}{3} = 1.33$$


$$g_{avg}(\text{Lo-skewed}) = \frac{g_u + g_d}{2} = 1.388$$

$$g_{avg}(\text{Hi-skewed}) = g_{avg} = 1.388$$

Figure 4: Rising, falling, and average logic effort for the unskewed, high-skewed and low-skewed NAND2 gate.


NOR2:

Unskewed - up

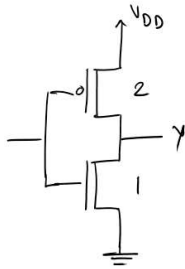


$$g_u = \frac{C_{in}}{C_{in}} = \frac{5}{3}$$

Unskewed - down

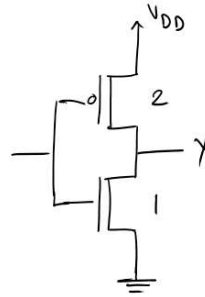

$$g_d = \frac{C_{in}}{C_{in}} = \frac{5}{3}$$


Lo-skewed-up

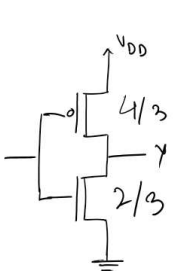

$$\frac{2R}{\frac{2R}{8/3} \times 2} = 4/3$$


$$g_u = \frac{8/3 + 1}{4/3 + 2/3} = 1.833$$

Lo-skewed-down

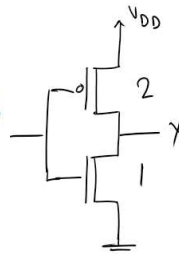


$$g_d = \frac{8/3 + 1}{3} = 1.22$$

Hi-skewed-up

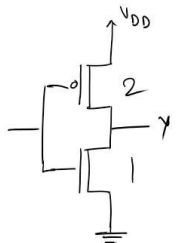

$$g_u = \frac{2/3 + 4}{3} = 1.556$$

Hi-skewed-down

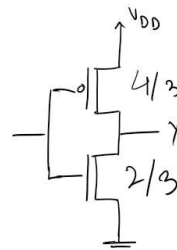

$$\frac{R}{\frac{R}{2/3}} = 2/3$$

$$g_d = \frac{2 + 4/3}{4/3 + 2/3} = 2.33$$

$$g_{avg}(\text{unskewed}) = \frac{5}{3} = 1.667$$

$$g_{avg}(\text{lo-skewed}) = \frac{g_u + g_d}{2} = 1.5275$$

$$g_{avg}(\text{hi-skewed}) = g_{avg} = 1.94465$$

Figure 5: Rising, falling, and average logic effort for the unskewed, high-skewed and low-skewed NOR2 gate.