

Experiment #4: Frequency Response and Bode Plots

4.1 Introduction:

The sinusoidal-steady-state response of a linear network is a sinusoid of the same frequency as the input excitation, but with different amplitude and phase angle. The ratio of the response-phasor to the excitation-phasor is frequency-dependent, and is called the **frequency-response function $H(\omega)$** of the network. Plots of $|H(\omega)|$ and $\angle H(\omega)$ versus frequency are often used to describe the frequency-selective characteristics of various linear networks such as feedback amplifiers and filters.

The frequency-response function $H(\omega)$ is closely related to the **transfer function $H(s)$** of the network, as $H(\omega) = H(s = j\omega)$. Both functions are useful in describing different aspects of behavior of linear networks. While $H(s)$ describes the pole-zero pattern (in the s-plane) of a network's transfer function, $H(\omega)$ describes the frequency-selective characteristics associated with such a pattern. Clearly, a change in the pole-zero patterns of $H(s)$ will yield a corresponding change in the frequency-response characteristics for the network.

To quickly visualize how the pole-zero pattern of the transfer function of a network affects the frequency-response characteristics, electrical engineers often use a **straight-line approximation** technique (known as the **Bode method**) to simplify the analysis and design of linear networks. Through quick analysis, the designer is then able to evaluate various possibilities before deciding on a suitable network. The Bode method is a conceptual technique that reduces the complete frequency-response characteristics to a sum of elementary straight-line approximations. The straight-line approximations of $|H(\omega)|$ in **dB** and $\angle H(\omega)$ in **degrees** versus frequency [**log scale**] are said to be the **asymptotic Bode plots** of the frequency response characteristics.

$$H(\omega)_{dB} = 20\text{Log}_{10}|H(\omega)|$$

This experiment examines the frequency-response characteristics of various linear networks. It also demonstrated the effectiveness of the Bode method in providing a quick visualization of the frequency-response for these networks.

4.2 Objectives:


- To draw the asymptotic Bode plots that approximates the frequency-response characteristics of various linear networks.
- To measure and plot the magnitude- and phase-frequency responses of the above-mentioned networks.
- To compare the asymptotic Bode plots and the practical measurements.

4.3 Prelab Assignment:

Step 1: Consider the network shown in **Fig (4.1)**.

- Derive the transfer function $H(s) = V_o/V_i$.
- Use **Graph (4.1)** to draw the asymptotic Bode plots for the frequency-response of the network.


Fig (4.1)

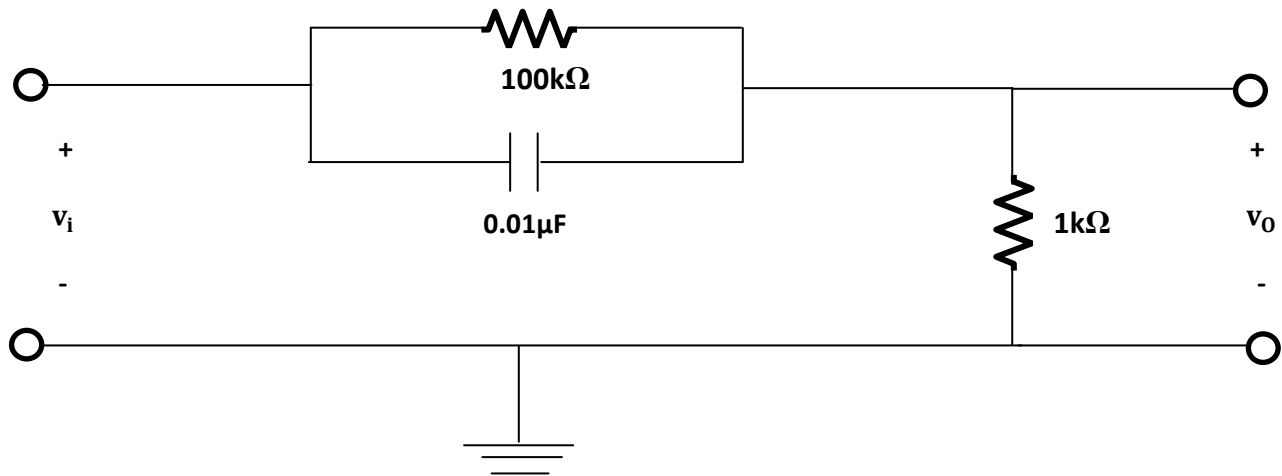

Step 2: Assume that the Op-Amp circuit in **Fig (4.2)** is working properly.

- Derive the transfer function $H(s) = V_o/V_i$.
- Use **Graph (4.2)** to draw the asymptotic Bode plots for the frequency-response of the Op-Amp circuit.

Fig (4.2)

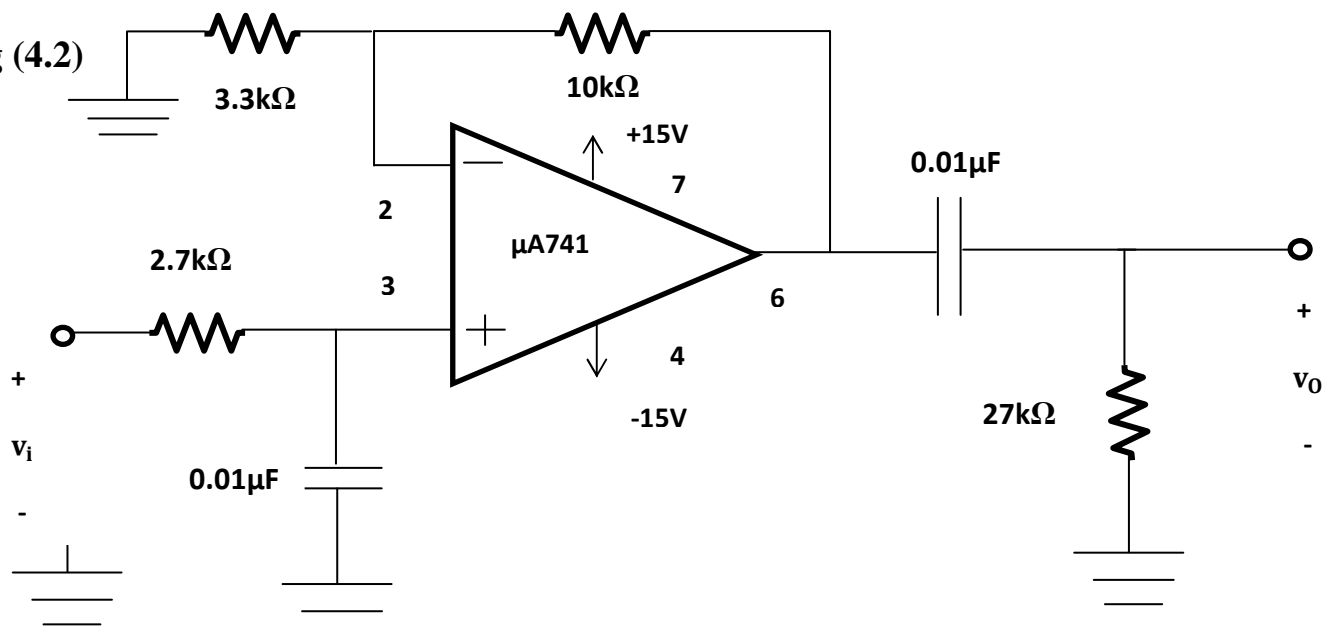

Step 3: Use **SPICE** software (please read Section 14.10 of Fundamentals of Electric Circuits 5th Edition) to plot the magnitude (**dB**) and phase (degrees) frequency-responses of each of the above circuits, for **10Hz ≤ f ≤ 100kHz**.

4.4 Procedure:

Part I: The Frequency Response Associated With [One Pole-One Zero] Transfer Function

Step 1: Connect the circuit shown in Fig (4.1). Connect channel (A) of the oscilloscope to display **V_i** and channel (B) of the oscilloscope to display **V_o**; set the trigger source → A. Adjust the controls of the function generator to provide a sinusoidal input voltage **V_i** of **5V (peak)** at a frequency of **100Hz**.

Step 2: Use the oscilloscope displays to measure the phase angle $\angle H(\omega)^0$, and use both DMMs to measure the dB-values of **V_i**, **V_o**, and the frequency, and evaluate the magnitude $|H(\omega)|$ in dB as: **$|H(\omega)|_{dB} = [V_o \text{ (in dB)} - V_i \text{ (in dB)}]$** .

Record your results in Table (4.1).

Step 3: Repeat as in Step 2 for each frequency setting in Table (4.1).

Step 4: Use **Graph (4.1)** to plot the magnitude $|H(\omega)|$ (dB) and phase $\angle H(\omega)^0$ versus frequency in Hz. Use your plot to determine the locations of the corner frequencies: **f_Z** and **f_P**.

f_Z = And **f_P** =

Part II: The Frequency Response Associated with [Two Poles-One Zero] Transfer Function

Step 5: Connect the circuit shown in **Fig (4.2)**. Connect channel (A) of the oscilloscope to display **V_i** and channel (B) of the oscilloscope to display **V_o**; set the trigger source → A. Adjust the controls of the function generator to provide a sinusoidal input voltage **V_i** of **0.5V (peak)** at a frequency of 100Hz.

Step 6: Repeat the measurements as in Step 2 and Step 3, and record your results in **Table (4.2)**.

Step 7: Use **Graph (4.2)** to plot the magnitude $|H(\omega)|$ (dB) and phase $\angle H(\omega)^0$ versus frequency in Hz. Use your plots to determine the locations of the corner frequencies: f_{p1} and f_{p2} .

$f_{p1} = \dots\dots\dots$ and
 $f_{p2} = \dots\dots\dots$