

Ryerson University
Department of Electrical and Computer Engineering
ELE734: LOW-POWER DIGITAL INTEGRATED CIRCUITS
Mid-Term Examination, November 2015
Duration: 1.5 hours

Student's Name: *Solution*

Student's Number: Section:

NOTES:

1. This is a **Closed Book** examination. No aids other than the approved calculators and **1** page of aid-sheet is allowed.
2. Answer all questions.
3. **No questions are to be asked** in the examination hall. If doubt exists as to the interpretation of any question, the student is urged to submit with the answer paper, a clear statement of any assumptions made.

<i>Question No.</i>	<i>Mark of each question</i>	<i>Mark obtained</i>
Q1	20	
Q2	20	
Q3	20	
Q4	20	
Total (Out of 80):		

15 min


Q1:

Design a static CMOS gate that has the following output.

$$Out = \overline{!(AB+C+D)}$$


- Draw the transistor-level schematic of your design. Sizing is not required. (8 marks)
- Draw stick diagram of the gate you designed (please clearly label metal, poly, n-diffusion and p-diffusion regions on your stick diagram). (8 marks)
- Estimate the area of the gate based on your stick diagram. (4 marks)

a) Pull down network

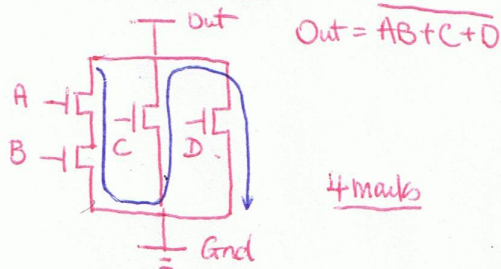


Pull up network
 
$$\begin{aligned} Out &= \overline{AB + C + D} \\ &= \overline{AB} \cdot \overline{C} \cdot \overline{D} \\ &= (\overline{A+B}) \cdot \overline{C} \cdot \overline{D} \end{aligned}$$



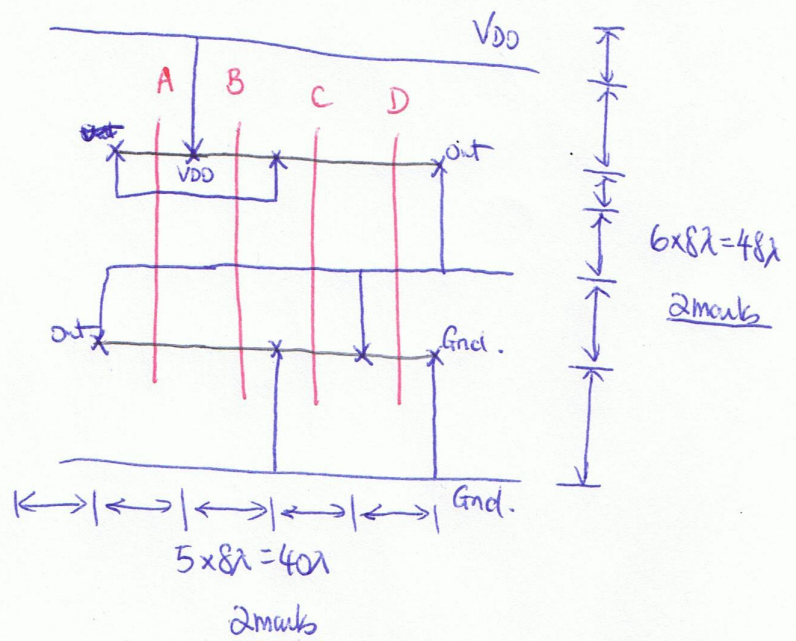b) 4 marks nmos network
4 marks pmos network



$$\begin{aligned} \text{Area} &= 48\lambda \times 40\lambda \\ &= 1920\lambda^2 \end{aligned}$$


Blank page

15min


 
Q2:

The on resistance of a unit nMOS is 15Kohms and the on resistance of a unit pMOS is 30Kohms. The following CMOS gate is driving a load (C_L) of 125fF.

- Assume the drain and source capacitance of each transistor is 0F. Size the gate to have a $t_{pdr} < 1900ps$ and $t_{pdf} < 1600ps$. (10 marks)
- Assume the drain, source, and gate capacitances of a unit transistor are all equal to 10fF, calculate the worst case pull-up and pull-down logic effort and the parasitic delay of the gate that you have just designed. (10 marks)



a)

  

$$\frac{30k}{A} * 125fF < 1900ps \quad \underline{2.5 \text{ marks}}$$

$$\left(\frac{15k}{B} + \frac{15k}{B} \right) * 125fF < 1600ps \quad \underline{2.5 \text{ marks}}$$

$$\frac{3750ps}{A} < 1900ps$$

$$\frac{30k}{B} * 125fF < 1600ps$$

$$\frac{3750ps}{1900ps} < A$$

$$\frac{3750ps}{B} < 1600ps$$

$$A > 1.97$$

$$\frac{3750ps}{1600ps} < B$$


$$A = 2 \quad \underline{2.5 \text{ marks}}$$

$$B > 2.34$$


$$B = 3 \quad \underline{2.5 \text{ marks}}$$

Blank page

b) Worst case pull down logic effort

 


2 marks

 

$$\begin{aligned} t_{pdf} &= 30fF \cdot 5K + 10K(30 + 40 + 50 \cdot h) fF \\ &= 150ps + 700ps + 500ps \cdot h \\ &= 850ps + 500ps \cdot h \end{aligned}$$

3 marks

② Unloaded inverter

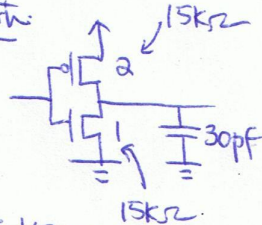


$$\begin{aligned} \text{delay} &= 30fF \cdot 15K \\ &= 450ps \end{aligned}$$

2 marks

$$df = \frac{850ps + 500ps \cdot h}{450ps} = 1.89 + 1.11h$$

Worst case pull up logic effort

 


$$\begin{aligned} t_{pdr} &= 30fF \cdot 15K + 15K(30fF + 40fF + 50fF \cdot h) \\ &= 450ps + 1050ps + 750ps \cdot h \\ &= 1500ps + 750ps \cdot h \end{aligned}$$

3 marks



$$dr = \frac{1500ps + 750ps \cdot h}{450ps} = 3.33 + 1.66h$$

Q3: Assume $V_t = 0.3V$, $V_b = -0.1V$, $V_{dd} = 1.2V$.

 a) Calculate I_{ds} for the following transistor using the Long-Channel model. (10 marks)




  b) Calculate subthreshold current for the following transistor. (10 marks)



The transistor is in saturation - 4 marks
 
$$\begin{aligned}
 I_{ds} &= \frac{\beta}{2} V_{GT}^2 \\
 &= \frac{1048}{2} (1.2 - 0.1 - 0.3)^2 \\
 &= \frac{1048}{2} 0.8^2 \\
 &= 335.36 \mu A. \quad - 6 \text{ marks}
 \end{aligned}$$



The transistor is in cutoff - 4 marks

$$\begin{aligned}
 &0.1 \mu A 10 \frac{0.01V + 100mV/V \cdot (1.0 - 1.2) - 0.082 \cdot 0.2V}{100mV/V} (1 - e^{-\frac{1.0}{26mV}}) \\
 &= 0.1 \mu A 10 \frac{0.01V - 20mV - 0.0166V}{100mV/V} (1 - e^{-\frac{1.0}{26mV}}) \\
 &= 0.1 \mu A 10^{-0.266} (1 - e^{-38.46}) \\
 &= 0.054 \mu A \quad - 6 \text{ marks}
 \end{aligned}$$


Blank page

20 min

Q4:

a) Calculate the optimum path delay for the following circuit and the value of x, y, and z in order to achieve the optimum delay. (inverter: $g=1, p=1$; 2-input nand: $g=4/3, p=2$; 2-input nor: $g=5/3, p=2$; 4-input nand: $g=6/3, p=4$). (10 marks)

 b) What will be the optimal delay if you can insert additional inverters at the end of the 4-input nand gate? Please also calculate the value of x, y, z, and the size of each additional inverter stage. (10 marks)



a) $H = \frac{250}{1} = 250$ - 1 mark
 $G = 1 \cdot \frac{4}{3} \cdot \frac{5}{3} \cdot \frac{6}{3} = 4.44$ - 1 mark
 $B = 2 \cdot 2 \cdot 3 \cdot 1 = 12$ - 1 mark
 $(GBH)^{1/4} = (4.44 \cdot 12 \cdot 250)^{1/4}$ - 1 mark
 $= 10.746$
 $10.746 \times 4 + 1 + 2 + 2 + 4$ - 2 marks
 $= 51.984$

$\frac{2 \cdot x}{1} = 10.746 \Rightarrow x = 5.373$ - 1 mark

$2 \cdot \frac{4}{3} \cdot \frac{y}{x} = 10.746 \Rightarrow y = 21.65$ - 1 mark

$3 \cdot \frac{5}{3} \cdot \frac{z}{y} = 10.746 \Rightarrow z = 46.53$ - 1 mark

$\frac{6}{3} \cdot \frac{250}{z} = 10.746 \Rightarrow 250 = 250 \checkmark$

1 mark for effort.

b) $(GBH)^{1/n} = (13333.33)^{1/n} = 3.59$ - 2 marks

$\log 3.59 = \frac{1}{n} \log (13333.33)$

$n = \frac{\log (13333.33)}{\log 3.59}$

$n = 7.43$ stages - 1 mark

Version-1

$(GBH)^{1/8} = (13333.33)^{1/8} = 3.28$ - 2 marks

$2 \cdot \frac{x}{1} = 3.28 \Rightarrow x = 1.64$

$2 \cdot \frac{4}{3} \cdot \frac{y}{x} = 3.28 \Rightarrow y = 2.017$

$3 \cdot \frac{5}{3} \cdot \frac{z}{y} = 3.28 \Rightarrow z = 1.323$

$\frac{6}{3} \cdot \frac{a}{z} = 3.28 \Rightarrow a = 2.17$ - 1 mark

$1 \cdot \frac{b}{a} = 3.28 \Rightarrow b = 7.18$ - 1 mark


$1 \cdot \frac{c}{b} = 3.28 \Rightarrow c = 23.35$ - 1 mark

$1 \cdot \frac{d}{c} = 3.28 \Rightarrow d = 76.57$ - 1 mark

$1 \cdot \frac{250}{d} = 3.28 \Rightarrow 250 \approx 257$ check \checkmark

8 stages
 $3.28 \times 8 + 1 + 2 + 2 + 4 + 4$
 $= 39.24$

 7 stages
 $(13333.33)^{1/7} \times 7 + 1 + 2 + 2 + 4 + 4$
 $= 43.27$
 39.18



Blank page

Version 2 7 stages

$$(GBH)^{1/7} = (13333.33)^{1/7} = 3.88398 \quad - 2 \text{ marks}$$

$$\left. \begin{array}{l} 2 \cdot \frac{x}{1} = 3.88 \Rightarrow x = 1.94 \\ 2 \cdot \frac{4}{3} \cdot \frac{y}{x} = 3.88 \Rightarrow y = 2.82 \\ 3 \cdot \frac{5}{3} \cdot \frac{z}{y} = 3.88 \Rightarrow z = 2.197 \end{array} \right\} - 1 \text{ mark}$$

$$\frac{6}{3} \cdot \frac{a}{z} = 3.88 \Rightarrow a = 4.2367 \quad - 1 \text{ mark}$$

$$1 \cdot \frac{b}{a} = 3.88 \Rightarrow b = 16.4857 \quad - 1 \text{ mark}$$

$$1 \cdot \frac{c}{b} = 3.88 \Rightarrow c = \cancel{64.46} 64.367 \quad - 1 \text{ mark}$$

$$1 \cdot \frac{250}{c} = 3.88 \Rightarrow 250 \approx 250$$

1 mark for effort

Formulae and Constants

$$\beta = 1048 \mu A / V^2$$

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{Cutoff} \\ \beta(V_{GT} - V_{ds}/2)V_{ds} & V_{ds} < V_{dsat} & \text{Linear} \\ \frac{\beta}{2}V_{GT}^2 & V_{ds} > V_{dsat} & \text{Saturation} \end{cases}$$

$$\eta = 100 mV / V$$

$$k_{\lambda} = 0.083$$

$$S = 100 mV / V$$

$$v_T = 26 mV$$

$$I_{off} = 0.1 \mu A$$

$$I_{ds} = I_{off} 10^{\frac{V_{gs} + \eta(V_{ds} - V_{dd}) - k_{\lambda} V_{sb}}{S}} \left(1 - e^{\frac{-V_{ds}}{v_T}}\right)$$