## Midterm



Time Limit: 1:30:00

Time Left:Time Exceeded

Vatsal Shreekant: Attempt 1

## Page 1:



Design a static CMOS gate that has the following output.

Out = 
$$!((A*B)+(C*D))$$

- a) Draw the transistor-level schematic of your design. Sizing is not required. (8 marks)
- b) Draw stick diagram of the gate that you have designed (please minimize layout area by maximizing diffusion sharing and clearly label metal, poly, n-diffusion and p-diffusion regions on your stick diagram). (8 marks)
- c) Estimate the area of the gate based on your stick diagram. (4 marks)



Add a File Record Audio Record Video

| VS\_Q\_1.pdf (626.7 KB) 
| Source: My Computer

Assume the on-resistance of a unit nMOS is 15Kohms and the on-resistance of a