




**Faculty of Engineering and Architectural
Science**

Department of Electrical and Computer Engineering

Course Number	ELE 734
Course Title	Low Power Digital Integrated Circuits
Semester/Year	7 th Semester, 4 th Year
Lab No	2
Instructor Name	Andy Ye
Section No	3

Submission Date	10/25/2020
Due Date	10/25/2020

Name	Student ID	Signature*
John Tiglao	500751493	

****By signing above, you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result***


in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at:

www.ryerson.ca/senate/current/pol60.pdf


Introduction

The objective of this lab is to investigate the characteristics of the CMOS inverter. The static and dynamic behavior of the gate were looked into, and can be used to further explore logic gates, such as NAND, NOR, and XOR, or subsystems, such as adders and multipliers. DC analysis was first used to understand the static behavior and from it was able to obtain the transfer function, switching threshold, and the noise margin. Using transient analysis, the delay and load driving capability were also investigated. The layout of a CMOS inverter was also created and compared to the equal schematic-level through its static and dynamic results.


Schematic of CMOS Inverter

 


Schematic of Testbench

 

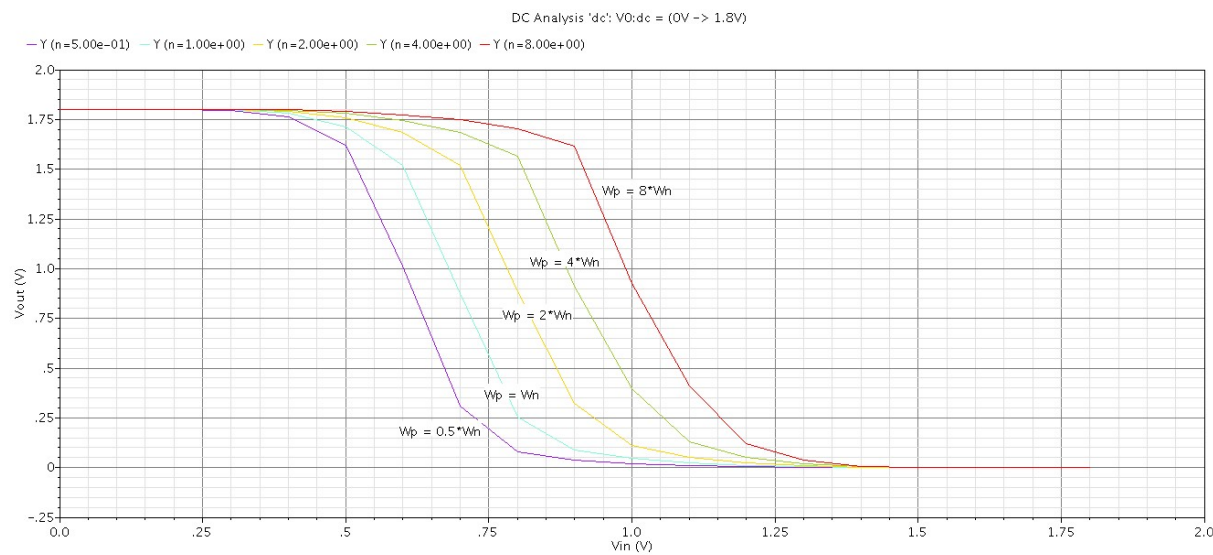
Static Analysis of CMOS Inverter, 0V -> 1.8V




Static Analysis of CMOS Inverter, n = 4

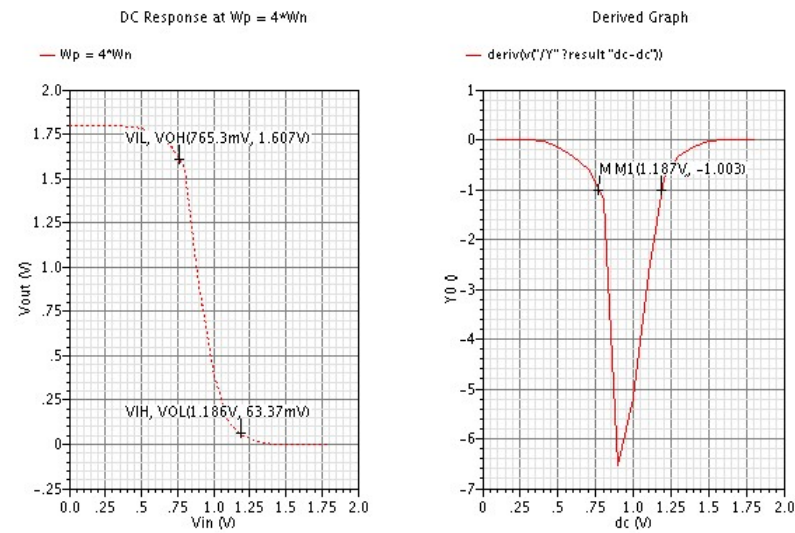


Dynamic Analysis of CMOS Inverter

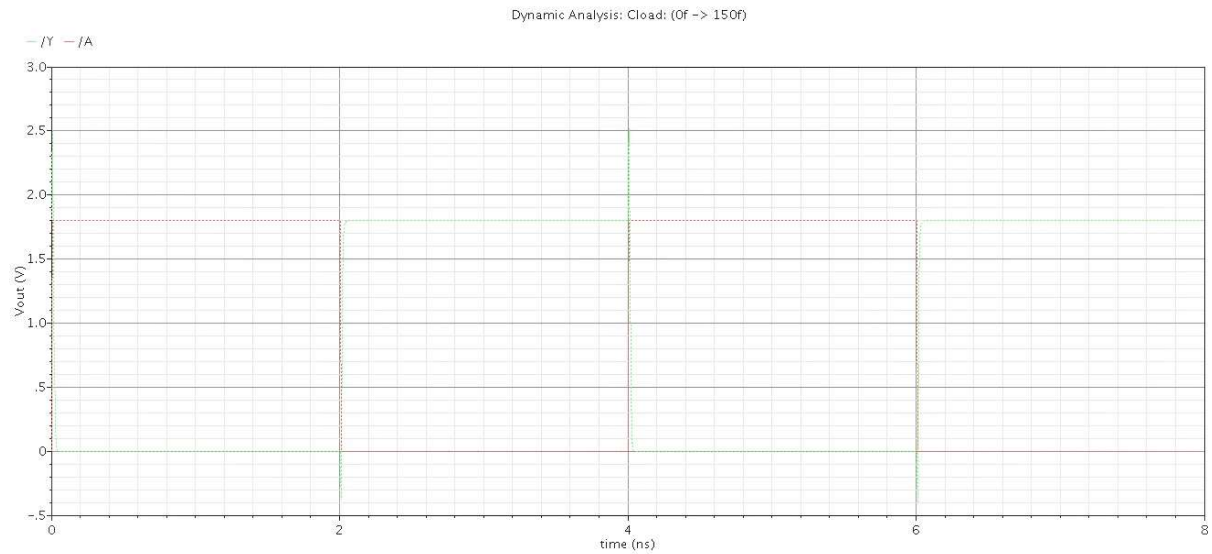


Physical View of CMOS Inverter Layout

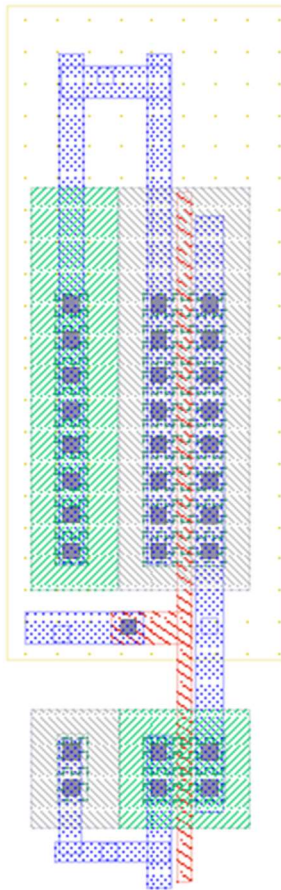


Extracted View of CMOS Inverter Layout

 

 Static Analysis of Schematic vs. Extracted



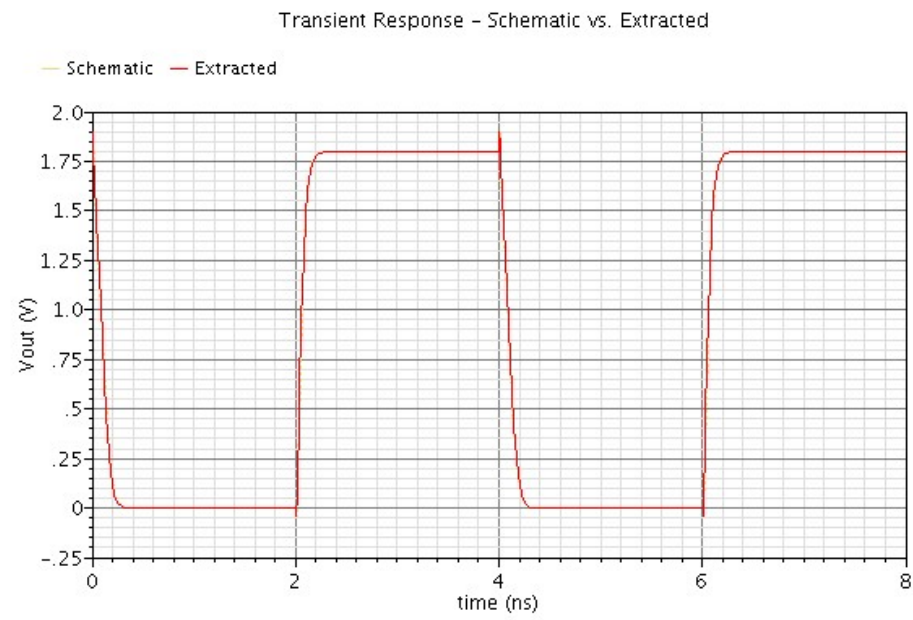Dynamic Analysis of Schematic vs. Extracted



Conclusion

In conclusion, this lab experiment studied different types of characteristics of a CMOS inverter, then further studied the layout of a CMOS inverter. The static and dynamic simulations were analyzed through different types of tools and analysis, Transient, DC, and Parametric analysis. From these analyses, a family of curves were created to find an ideal value for n (multiplier for the width of the PMOS). The ideal value for n was found to be 4 and used throughout the lab. The static analysis was used on this ideal value to create its DC response and find the V_{IL} , V_{OH} , V_{IH} , and V_{OL} of the graph by first obtaining the derivative of the graph. The dynamic simulation was investigated using transient analysis for a capacitance from 0f to 150f. The physical view for the CMOS inverter was created and used to create the extracted view. The extracted view had the same analyses applied from before with and had its static compared to the same CMOS schematic. The graph shows the two types of ways to obtain the static simulations, schematic and extracted, and had returned the same graphs. This was further proved through the dynamic simulation which also appeared completely identical. Sizing PMOS twice as wide as the NMOS did not result in $V_M = V_{DD}/2$ because of the delay. Increasing the PMOS size relative to NMOS will both increase V_M and reduce the rise delay.